
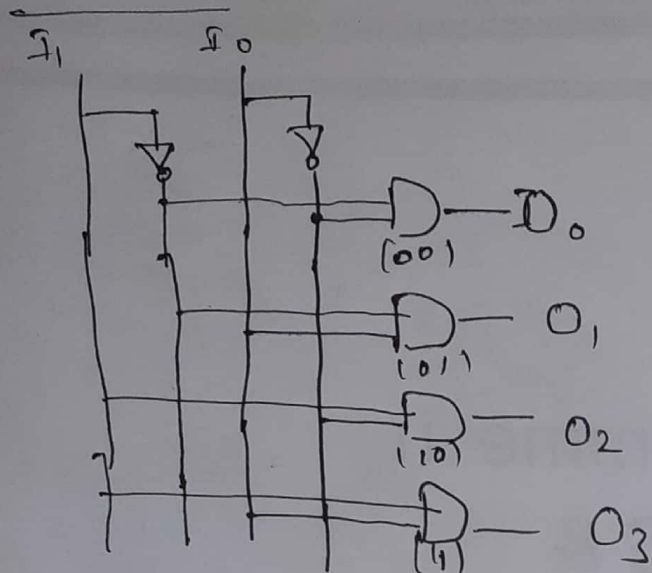




2x4 decoder

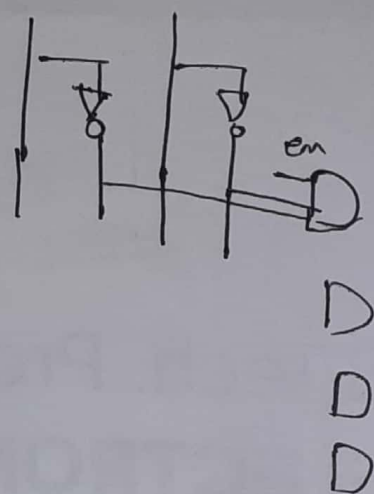


2x4 decoder with Enable




$$Y = AB' + A'C$$

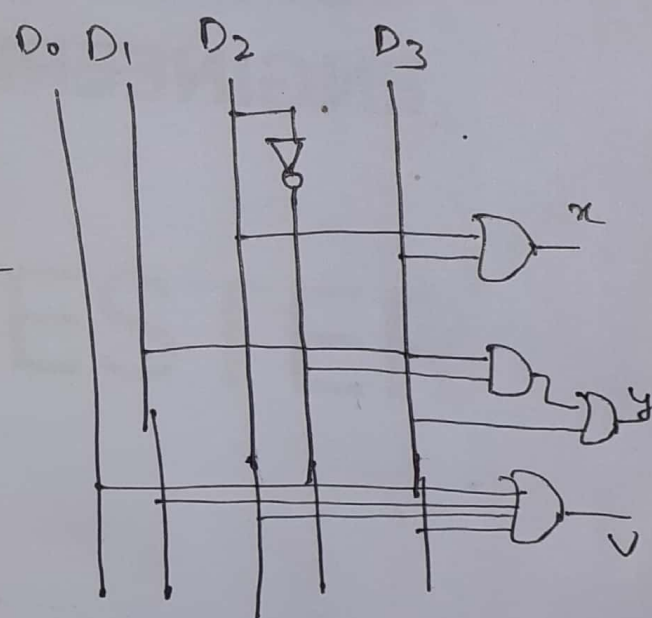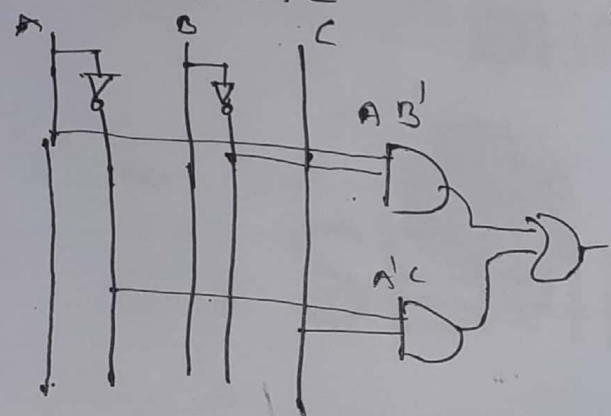



2x1 MUX

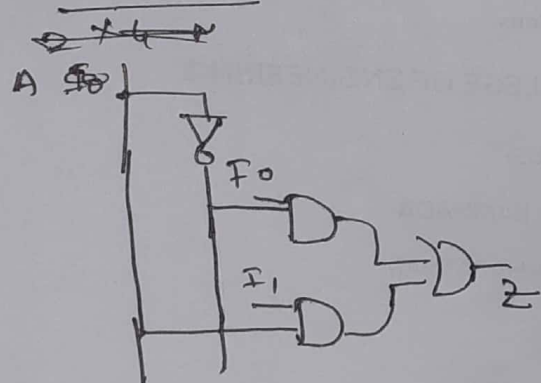


4x1 MUX

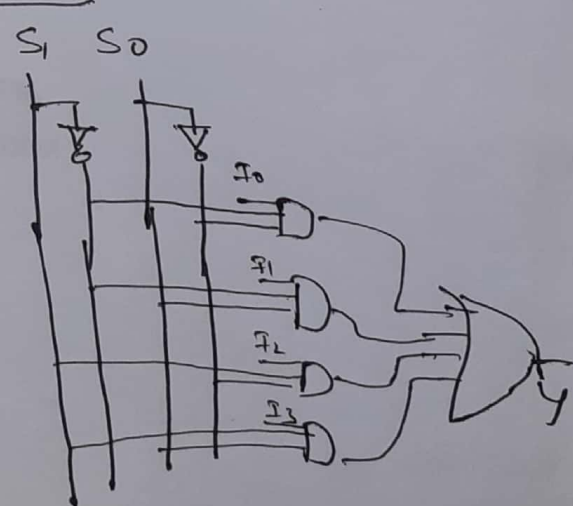


8x1 MUX using 2x1 MUX

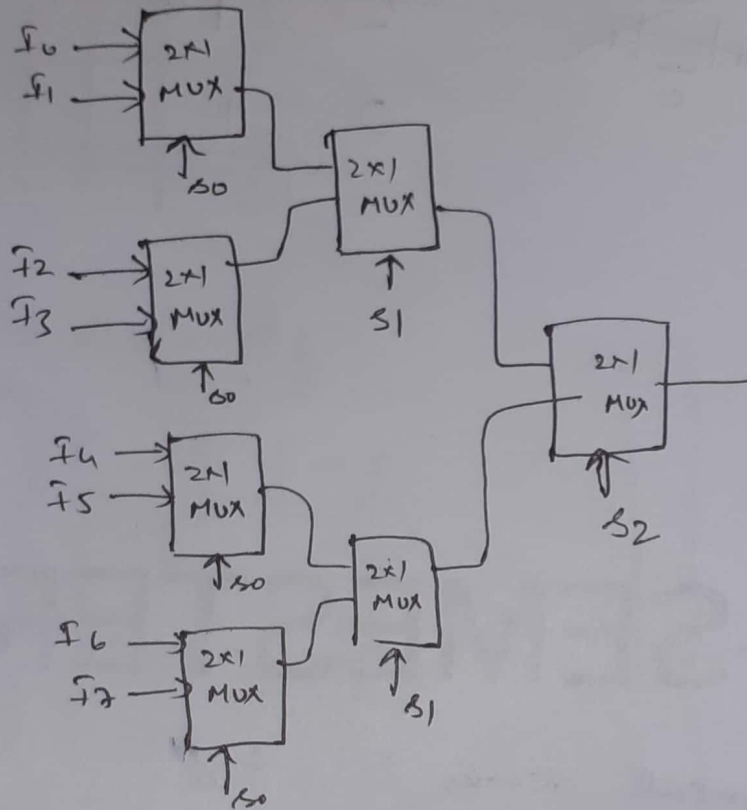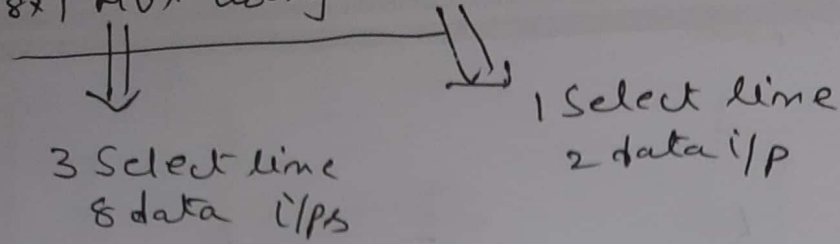

8x1 MUX using 4x1 MUX

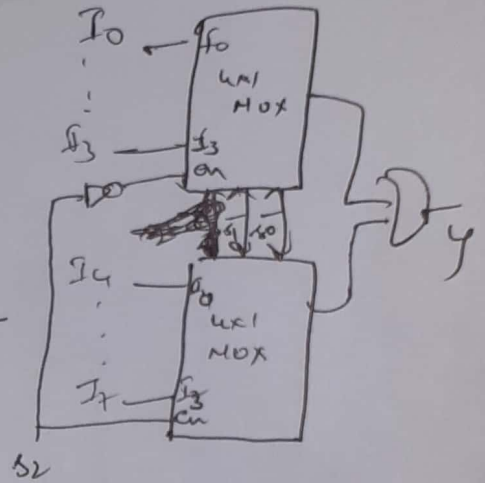

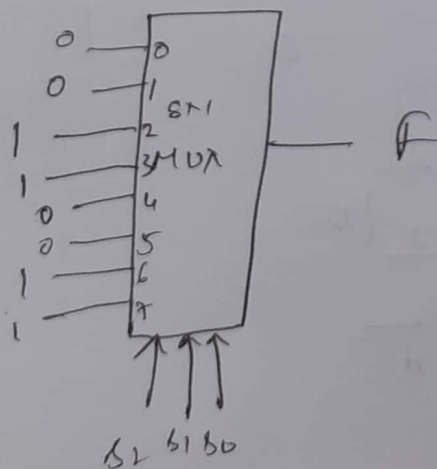using
Design a 8x1 MUX design a logic circuit to realize the following Boolean function $F(A, B, C) = \sum m(2, 3, 6, 7)$



$F(A, B, C) = \sum m(2, 3, 6, 7)$
using 8x1 MUX

Seven Segment decodes

