

Odd-Parity generator: ~


→ Consider the odd parity generator using an XOR gate and a NOT gate, shown in fig 4(a) below.

Let the 8-bit number $x_7x_6x_5x_4x_3x_2x_1x_0$ be equal to 01000001. This number has even parity.

It means that, when it is applied to an exclusive-OR (XOR) gate, it will produce an output of 0.

Because of the inverter, $x_8 = 1$ and the final 9-bit output is 1 01000001. Now it has odd parity.

 Thus, an XNOR gate can be used to generate Parity bits.



9-bit number with odd parity

Fig 4(a): odd-parity generation.

□ Code converters: ✓

→ A code converter is a logic circuit that changes data presented in one type of binary code to another type of binary code. The following are some of most commonly used code converters:

- (i) BCD to binary
- (ii) Binary to BCD
- (iii) Binary to Gray code
- (iv) Gray code to binary

□ BCD to binary converters: ✓

The steps involved in the BCD-to-binary conversion process are as follows:

1. The value of each bit in the BCD number is represented by a ^{decimal}~~binary~~ equivalent or weight.
2. All the binary weights of the bits that are 1s in the BCD are added.
3. The result of this addition is the binary equivalent of the BCD number.

→ Two-digit decimal values ranging from 00 to 09 can be represented in BCD by two 4-bit code groups. For example, 19_{10} is represented by as

$$\begin{array}{c} \text{1} \\ \hline 0001 \end{array} \quad \begin{array}{c} \text{9} \\ \hline 1001 \end{array}$$

The left-most four bit groups represents 10 and right-most four-bit group represents 9. That is, the left-most group has a weight of $10^1 = 10$

and the right-most group has a weight of $10^0 = 1$. The straight binary representation for decimal 19 is $19_{10} = 10011_2$. Fig 5(a) shows the block diagram of a two-digit BCD-to-binary converter.

The inputs to the converter are the two 4-bit code groups D_0, C_0, B_0, A_0 representing the 10^0 or units digit and D_1, C_1, B_1, A_1 representing 10^1 or tens digit of the decimal values.

→ Let $b_6, b_5, b_4, b_3, b_2, b_1, b_0$ be the outputs of the converter, the 7 bits of the binary equivalent of the decimal values. The binary equivalent of each BCD bit is a binary number representing the weight of that bit within the total BCD number. This is given in table-1(a)

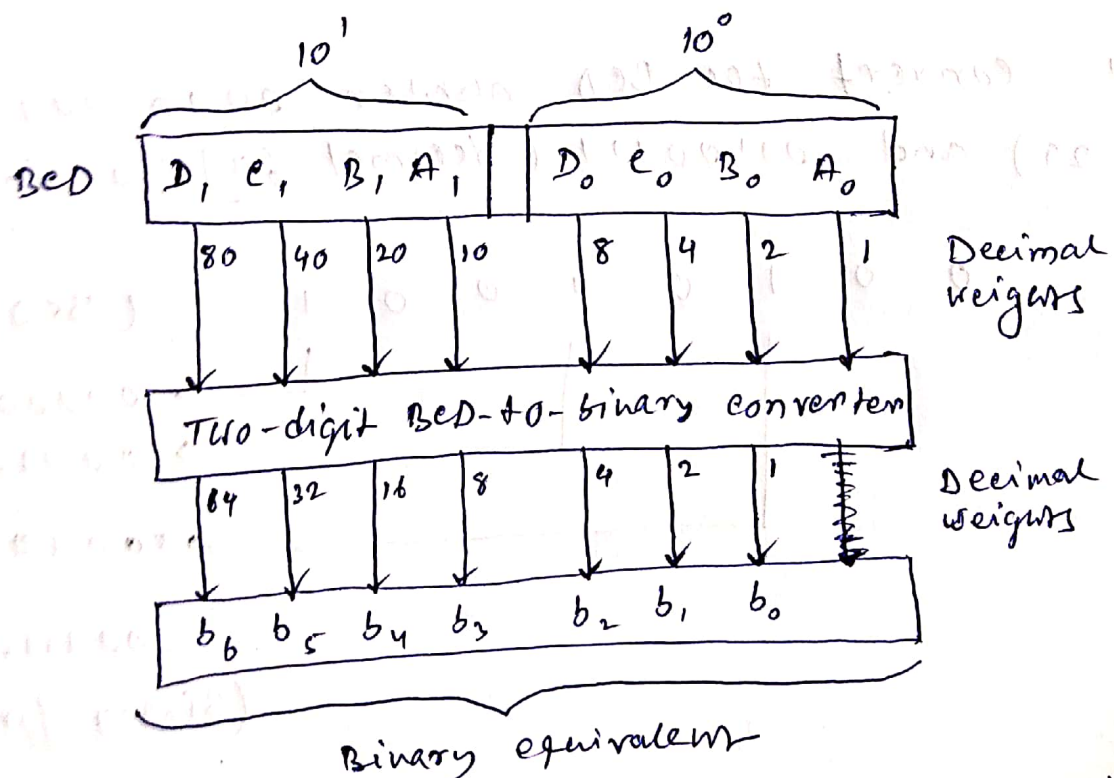


Fig: 5(a) Block diagram of a 2-digit BCD-to-binary converter.

BCD bit	BCD weight or decimal weight	binary equivalent or weight						
		b_6 (=64)	b_5 (=32)	b_4 (=16)	b_3 (=8)	b_2 (=4)	b_1 (=2)	b_0 (=1)
A_0	1	0	0	0	0	0	0	1
B_0	2	0	0	0	0	0	1	0
C_0	4	0	0	0	0	1	0	0
D_0	8	0	0	0	1	0	0	0
A_1	10	0	0	0	1	0	1	0
B_1	20	0	0	1	0	1	0	0
C_1	40	0	1	0	1	0	0	0
D_1	80	1	0	1	0	0	0	0


→ Using the weights, the BCD to binary conversion can be done easily by computing the binary sum of the binary equivalents or weights of those bits in the BCD representation that are 1s.

Ex.-1 Convert the BCD number 00101001 (decimal 29) and 01100111 (decimal 67) to binary.

⇒

0	0	1	0	1	0	0	1	(BCD)
								→ 00000001 1
								→ 00010000 8
								→ 00010100 20
								→ 0011101 29

(Binary for 29)

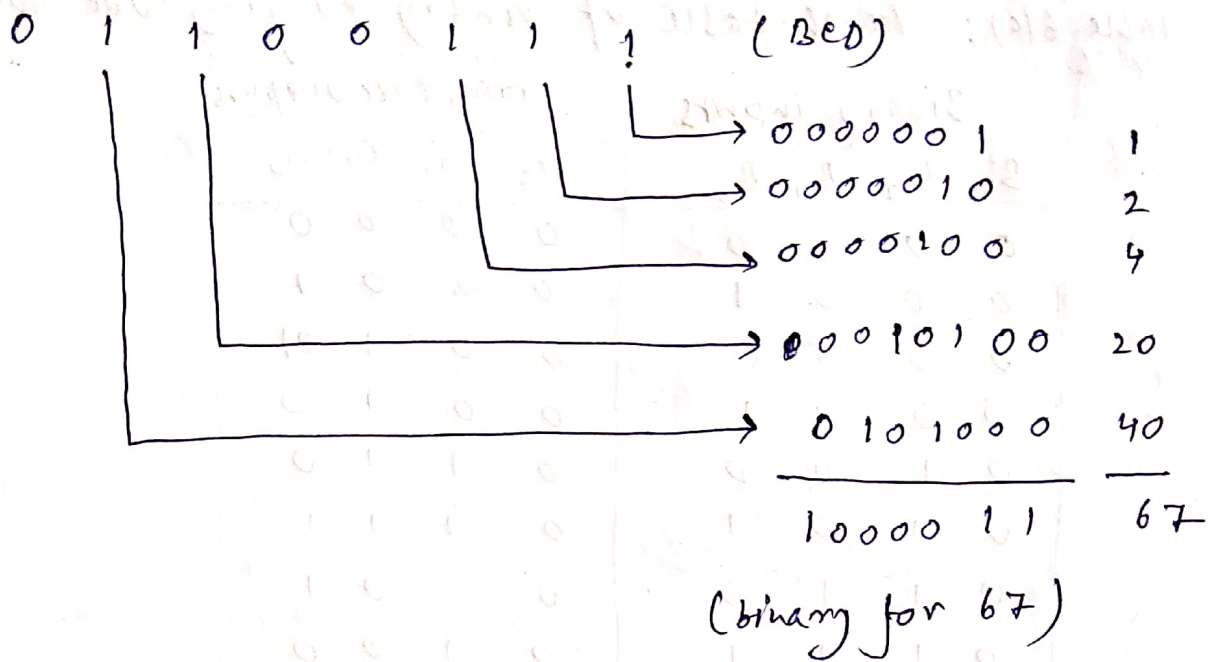

□ Binary-to-Gray code converters: ✓

The block diagram of a 4-bit binary-to-gray code converter is shown in fig 6(a). It has four inputs (B_3, B_2, B_1, B_0) representing 4-bit binary numbers and four outputs (G_3, G_2, G_1, G_0) representing 4-bit gray code. The truth table for the binary-to-gray code converter is shown in table 6(a).

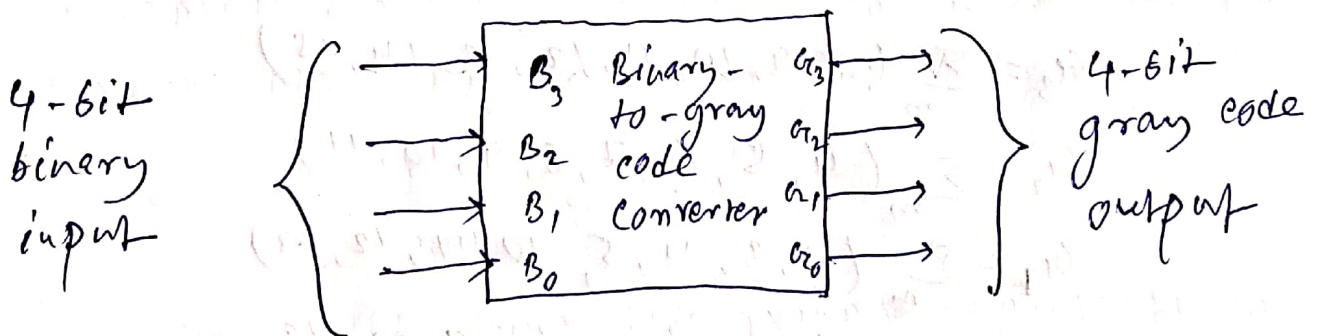


Fig 6(a): Block diagram of 4-bit binary-to-gray code converter.

Table 6(a): Truth-table of binary to gray code converters.

Binary inputs				Gray code outputs			
B_3	B_2	B_1	B_0	G_3	G_2	G_1	G_0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	0
0	0	1	1	0	0	1	1
0	1	0	0	0	1	1	0
0	1	0	1	0	1	1	1
0	1	1	0	0	1	0	1
0	1	1	1	0	1	0	0
1	0	0	0	1	1	0	0
1	0	0	1	1	1	0	1
1	0	1	0	1	1	1	1
1	0	1	1	1	1	1	0
1	1	0	0	1	0	1	0
1	1	0	1	1	0	1	1
1	1	1	0	1	0	0	1
1	1	1	1	1	0	0	0

From the truth table shown in table 6(a), the logic expressions for the gray code outputs can be written as:

$$G_3 = \sum_m (8, 9, 10, 11, 12, 13, 14, 15)$$

$$G_2 = \sum_m (4, 5, 6, 7, 8, 9, 10, 11)$$

$$G_1 = \sum_m (2, 3, 4, 5, 10, 11, 12, 13)$$

$$G_0 = \sum_m (1, 2, 5, 6, 9, 10, 13, 14)$$

The above expressions can be simplified using K-map method as shown in Table 6(b) - 6(e).

$B_1 B_0$	$B_3 B_2$			
	00	01	11	10
00	0	0	1	1
01	0	0	1	1
11	0	0	1	1
10	0	0	1	1

6(b): K-map of G_3

$B_1 B_0$	$B_3 B_2$			
	00	01	11	10
00	0	1	0	1
01	0	1	0	1
11	0	1	0	1
10	0	1	0	1

6(c): K-map of G_2

$B_1 B_0$	$B_3 B_2$			
	00	01	11	10
00	0	1	1	0
01	0	1	1	0
11	1	0	0	1
10	1	0	0	1

6(d): K-map of G_1

$B_1 B_0$	$B_3 B_2$			
	00	01	11	10
00	0	0	0	0
01	1	1	1	1
11	0	0	0	0
10	1	1	1	1

6(e): K-map of G_0

→ From table 6(b), $G_3 = B_3$ — (i)

From table 6(c), $G_2 = B_2 \bar{B}_3 + B_3 \bar{B}_2$ — (ii)

From table 6(d), $G_1 = B_2 \bar{B}_1 + \bar{B}_2 B_1$ — (iii)

From table 6(e), $G_0 = \bar{B}_1 B_0 + B_1 \bar{B}_0$ — (iv)

→ Now, the above expressions can be implemented using

XOR gates as shown in fig 6(b) below.

 


Fig 6(b): Logic diagram of 4-bit binary-to-gray code converter.

Gray-to-binary converters:

→ The block diagram of a 4-bit gray-to-binary converter is shown in fig 6(a). It has four inputs (G_3, G_2, G_1, G_0) representing 4-bit gray code and four outputs (B_3, B_2, B_1, B_0) representing 4-bit binary number. The truth table for the gray code-to-binary converter is shown in table 6(a).

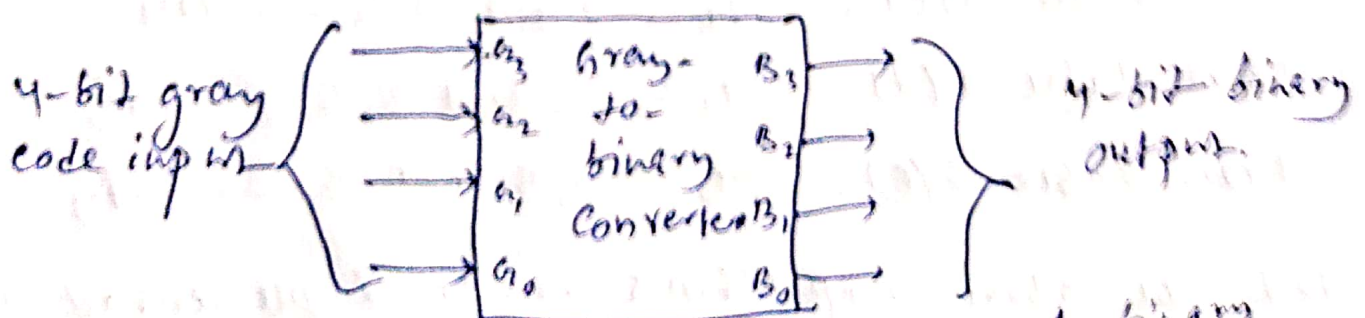


Fig 6(a): Block diagram of 4-bit gray-to-binary converter.

→ The truth table of the gray code-to-binary converter is shown in table 6(a).

Table 6(a): Truth table of gray code-to-binary converter.

Gray code output				Binary output			
G_3	G_2	G_1	G_0	B_3	B_2	B_1	B_0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	1
0	0	1	1	0	0	1	0
0	1	0	0	0	1	1	1
0	1	0	1	0	1	1	0
0	1	1	0	0	1	0	0
0	1	1	1	0	1	0	1
1	0	0	0	1	1	1	1
1	0	0	1	1	1	1	0
1	0	1	0	1	1	0	0
1	0	1	1	1	1	0	1
1	1	0	0	1	0	0	0
1	1	0	1	1	0	0	1
1	1	1	0	1	0	1	1
1	1	1	1	1	0	1	0

→ From the above truth table, the logic expressions for the binary outputs can be written as:

$$B_3 = \sum_m (8, 9, 10, 11, 12, 13, 14, 15)$$

$$B_2 = \sum_m (4, 5, 6, 7, 8, 9, 10, 11)$$

$$B_1 = \sum_m (2, 3, 4, 5, 8, 9, 14, 15)$$

$$B_0 = \sum_m (1, 2, 4, 7, 8, 11, 13, 14)$$

The above expressions can be simplified using K-map method as shown in table 6(b) - 6(e).

$a_1 a_0 \backslash a_3 a_2$	00	01	11	10
00	0	0	1	1
01	0	0	1	1
11	0	0	1	1
10	0	0	1	1

Table: 6(b)

$a_1 a_0 \backslash a_3 a_2$	00	01	11	10
00	0	1	0	1
01	0	1	0	1
11	0	1	0	1
10	0	1	0	1

Table: 6(c)

$a_1 a_0 \backslash a_3 a_2$	00	01	11	10
00	0	1	0	1
01	0	1	0	1
11	1	0	1	0
10	1	0	1	0

Table: 6(d)

$a_1 a_0 \backslash a_3 a_2$	00	01	11	10
00	0	1	0	1
01	1	0	1	0
11	0	1	0	1
10	1	0	1	0

Table: 6(e)

→ From table 6(b), $B_2 = a_2$ —(i)

From table 6(c), $B_2 = \bar{a}_3 a_2 + a_3 \bar{a}_2 = a_3 \oplus a_2$ —(ii)

From table 6(d), $B_1 = \bar{a}_3 \bar{a}_2 a_1 + \bar{a}_3 a_2 \bar{a}_1 + a_3 a_2 a_1 + a_3 \bar{a}_2 \bar{a}_1$

~~From table 6(e)~~

or $B_1 = \bar{a}_3 (\bar{a}_2 a_1 + a_2 \bar{a}_1) + a_3 (a_2 a_1 + \bar{a}_2 \bar{a}_1)$

$$= \bar{a}_3 (a_2 \oplus a_1) + a_3 (\overline{a_2 \oplus a_1})$$

$$= a_3 \oplus a_2 \oplus a_1$$

$$= a_3 \oplus B_2 \text{ —(iii) } [\because B_2 = a_3 \oplus a_2]$$

From table 6(e),

$$B_0 = \bar{a}_3 \bar{a}_2 \bar{a}_1 a_0 + \bar{a}_3 \bar{a}_2 a_1 \bar{a}_0 + \bar{a}_3 a_2 \bar{a}_1 \bar{a}_0 + \bar{a}_3 a_2 a_1 a_0$$

$$+ a_3 \bar{a}_2 \bar{a}_1 a_0 + a_3 \bar{a}_2 a_1 \bar{a}_0 + a_3 a_2 \bar{a}_1 \bar{a}_0 + a_3 a_2 a_1 a_0$$

$$= \bar{a}_3 \bar{a}_2 (\bar{a}_1 a_0 + a_1 \bar{a}_0) + a_3 a_2 (\bar{a}_1 a_0 + a_1 \bar{a}_0)$$

$$+ \bar{a}_1 \bar{a}_0 (\bar{a}_3 a_2 + a_3 \bar{a}_2) + a_1 a_0 (\bar{a}_3 a_2 + a_3 \bar{a}_2)$$

$$= \bar{a}_3 \bar{a}_2 (a_1 \oplus a_0) + a_3 a_2 (a_1 \oplus a_0)$$

$$+ \bar{a}_1 \bar{a}_0 (a_3 \oplus a_2) + a_1 a_0 (a_3 \oplus a_2)$$

$$= (a_1 \oplus a_0) (\bar{a}_3 \bar{a}_2 + a_3 a_2) + (a_3 \oplus a_2) (\bar{a}_1 \bar{a}_0 + a_1 a_0)$$

$$= (a_1 \oplus a_0) (\overline{a_3 \oplus a_2}) + (a_3 \oplus a_2) (\overline{a_1 \oplus a_0})$$

$$= a_0 \oplus a_1 \oplus a_2 \oplus a_3$$

$$= a_0 \oplus B_1 \text{ —(iv)}$$

Now the above expressions can be implemented using ~~XNO~~ XOR gates as shown in fig 6(b).

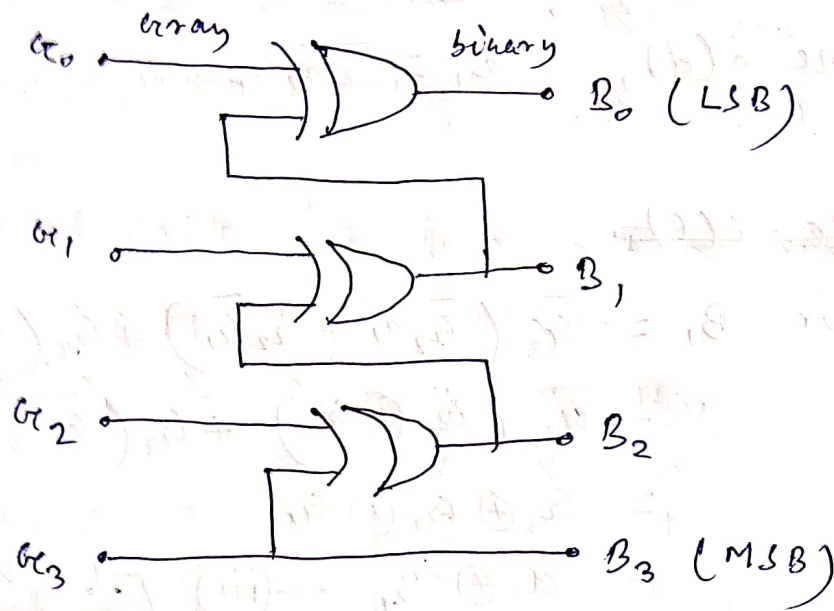


Fig 6(b): Logic diagram of 4-bit gray code-to-binary converter.

□ Priority Encoder: ✓

- A priority encoder is an encoder that includes the priority function. The operation of the priority encoder is such that if two or more inputs are equal to 1 at the same time, the input having the highest priority will take precedence.
- The truth table of four-input priority encoder is given in table below.
- The x_i are don't care conditions that designate the fact that the binary values they represent may be equal to 0 or 1.

→ Inputs D_3 has the highest priority; so regardless of the values of the other inputs, when this input is 1, the output $Y_2 Y_1$ is 11 (i.e. 3).

Table: Truth table of a four-input priority encoder

Inputs				Outputs		
D_0	D_1	D_2	D_3	Y_2	Y_1	V
0	0	0	0	X	X	0
1	0	0	0	0	0	1
X	1	0	0	0	1	1
X	X	1	0	1	0	1
X	X	X	1	1	1	1

→ D_2 has the next priority level. The output is 10 if $D_2=1$ and $D_3=0$, irrespective of the values of the other two lower priority inputs.

The output for D_1 is generated only if higher priority inputs are 0, and so on down the priority level. A valid output indicator, V is equal to 0, and the other two outputs of the circuit are not used.

set to 1 only when one or more of the inputs are equal to 1. If all the inputs are 0, V is equal to 0, and the other two outputs of the circuit are not used.

IC 74147 and IC 74148 are some of the priority encoder ICs.