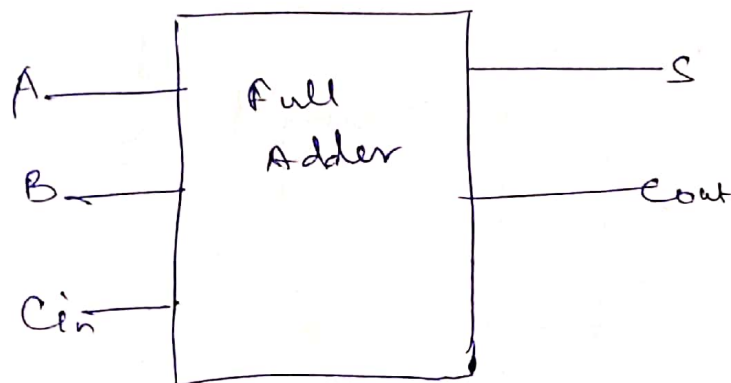


Full Adder

=> A half-adder has two 1-bit inputs and there is no provision to add any carry which could have been generated from lower bit order conditions.

=> The limitation of half-adder circuit is overcome in Full-adder.

=> The full adder is a Combinational logic circuit that has the provision to add a carry.



Inputs			Sum (S)	Carry (Cout)
A	B	Cin		
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

* 3 input bits, so total no. of combinations are $2^3 = 8$
* from 000 to 111

Process-1:-

To find the expression of Sum(S); we have to find the position having the value '1' in SOP.

$$\therefore S = \bar{A} \bar{B} \overset{\vee}{Cin} + \bar{A} B \bar{Cin} + A \bar{B} \bar{Cin} + A B \overset{\vee}{Cin}$$

(simplify using Boolean Algebra)

$$= (\bar{A} \bar{B} + \bar{A} B) Cin + (\bar{A} B + A \bar{B}) \bar{Cin}$$

$$= (\bar{A} \oplus B) Cin + (A \oplus B) \bar{Cin}$$

$$[\because \overline{X \cdot Y} = X \cdot \overline{Y} \quad \text{and} \quad X \cdot \overline{Y} = X \cdot \overline{Y}]$$

$$= A \oplus B \oplus Cin$$

[... considering $A \oplus B = X$ & $Cin = Y$
So, $\overline{X \cdot Y} + X \cdot \overline{Y} = X \oplus Y$]

$$\begin{aligned}
 \text{Now, } f_{\text{out}} Q &= \bar{A} B C_{in} + A \bar{B} C_{in} + A B \bar{C}_{in} + A B C_{in} \\
 &= \bar{A} B C_{in} + A \bar{B} C_{in} + A B (C_{in} + \bar{C}_{in}) \\
 &= \bar{A} B C_{in} + A \bar{B} C_{in} + A B [\because C_{in} + \bar{C}_{in} = 1] \\
 &= (\bar{A} B + A \bar{B}) C_{in} + A B \\
 &= (A \oplus B) C_{in} + A B \\
 &= A B + A C_{in} + B C_{in}
 \end{aligned}$$

Process - 2 :- By Using K-map Technique :-

** It is suggested in earlier classes also for simplification in SOP or POS forms please use K-map **

for S :-

		B C _{in}			
		00	01	11	10
A	0		1	1	1
		0	1	3	2
1	1	1		1	
		4	5	7	6

* Here, no groups are possible.
 * This particular type in K-map is known as check-board configuration.

* whenever this Configuration comes, we can write it is simply X-OR operation.


$$\therefore S = A \oplus B \oplus C_{in}$$

for c :-

	BCin			
	00	01	11	10
A				
0	0	1	3	2
1	4	5	7	6

$$C = AB + ACin + BCin$$

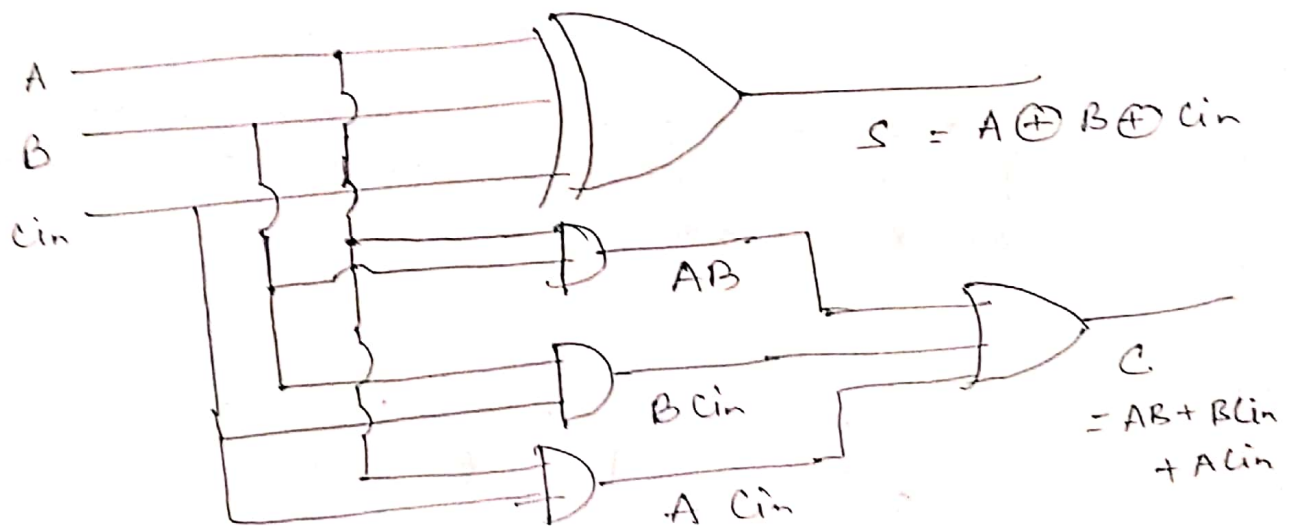Representation using ~~Half~~ Logic Gates :-



Full-Adder using Universal Logic:-

① NAND Logic:-

As, we have seen in half-adder logic,

$$S = \bar{x}y + x\bar{y} = \overline{x \cdot \bar{xy}} \cdot \overline{y \cdot \bar{xy}}$$

Here, we represented; input as A & B so,
for half-adder $S = \bar{A}B + A\bar{B} = \overline{A \cdot \bar{AB}} \cdot \overline{B \cdot \bar{AB}}$

Now, for full-adder;


$$S = \frac{A \oplus B}{x} \oplus \frac{C_{in}}{y}$$

$$= \overline{(A \oplus B) \cdot \overline{(A \oplus B)C_{in}}} \cdot \overline{C_{in} \cdot (A \oplus B)C_{in}}$$

$$C_{in} = C_{in}(A \oplus B) + AB = \overline{C_{in}(A \oplus B) \cdot AB}$$

[from De-Morgan's]

Similarly like half adder \Rightarrow

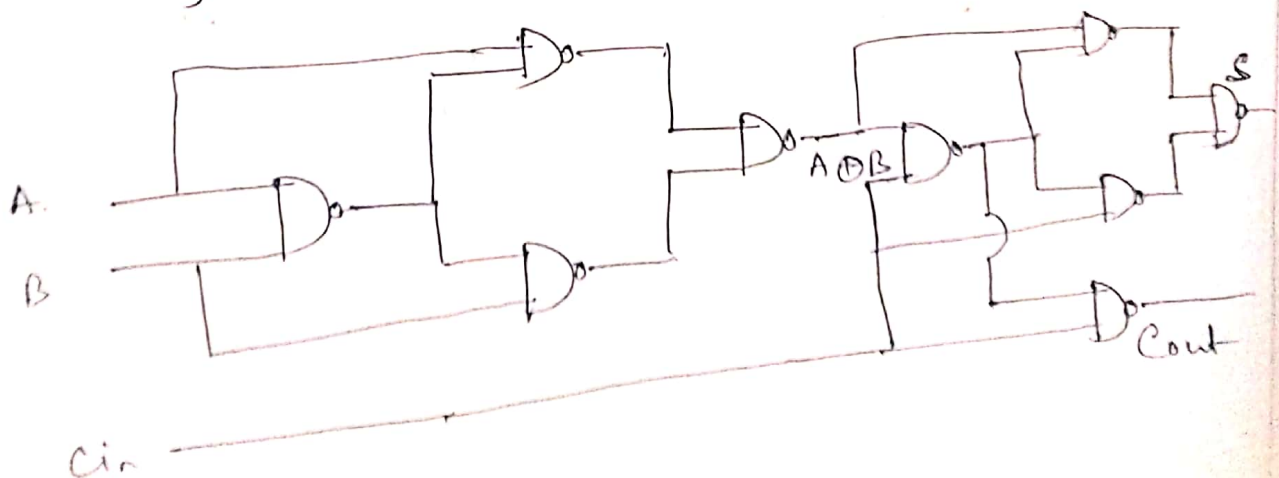

② NOR-Logic: - from half-adder \rightarrow

$$A \oplus B = \overline{A+B} + \overline{\bar{A}+\bar{B}}$$



For full-adder; $S = A \oplus B \oplus C_{in}$

$$= \overline{(A \oplus B) + C_{in}} + \overline{(\overline{A \oplus B}) + \overline{C_{in}}}$$

$$C_{out} = \overline{AB + C_{in}(A \oplus B)}$$

$$= \overline{A+B} + \overline{C_{in} + (A \oplus B)}$$

[using De-morgan's Theorem]

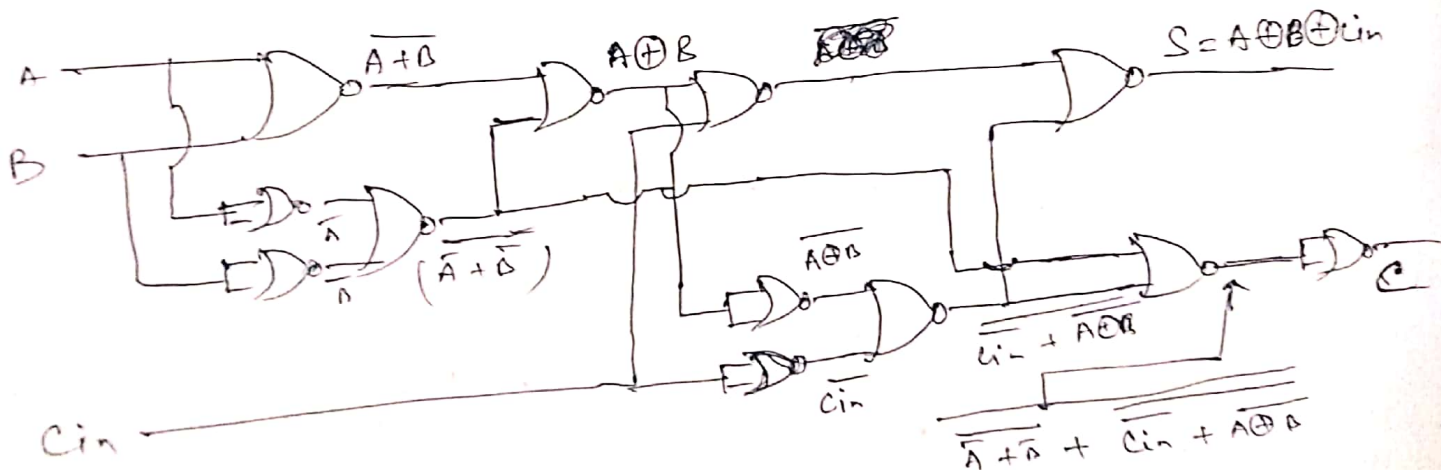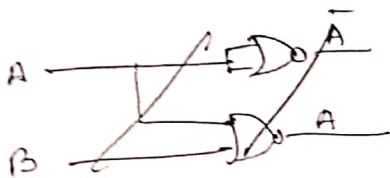

Full-adder using Half-adders:-

The boolean expression of full Adder are \rightarrow

$$\left. \begin{aligned} S_f &= C_{in} \oplus A \oplus B \\ \text{and } C_{out} &= AB + AC_{in} + BC_{in} \end{aligned} \right\} \text{--- (1)}$$

The boolean Expression for half-adder is

$$\left. \begin{aligned} S_h &= \cancel{C_{in}} \oplus A \oplus B \\ \text{and } C_h &= AB \end{aligned} \right\} \text{--- (2)}$$

$$\begin{aligned} \text{(1)} \Rightarrow S_f &= C_{in} \oplus \underline{A \oplus B} \\ &= \underline{C_{in} \oplus S_h} \end{aligned}$$

$$\text{and } C_{out} = AB + AC_{in} + BC_{in}$$

$$= AB + AC_{in} + BC_{in} (A + \bar{A}) \quad [\because A + \bar{A} = 1]$$

$$= \overbrace{AB + AC_{in} + ABC_{in}} + \bar{A}BC_{in}$$

$$= AB(1 + C_{in}) + AC_{in} + \bar{A}BC_{in}$$

$$= AB + AC_{in} + \bar{A}BC_{in}$$

$$= AB + AC_{in}(B + \bar{B}) + \bar{A}BC_{in} \quad [\because B + \bar{B} = 1]$$

$$= AB + ABC_{in} + A\bar{B}C_{in} + \bar{A}BC_{in}$$

$$= AB(1 + C_{in}) + C_{in}(A\bar{B} + \bar{A}B)$$

$$= AB + C_{in}(A \oplus B) \quad [\because 1 + C_{in} = 1]$$

$$= \underline{AB} + C_{in} \times S_h \quad [\because A \oplus B = S_h]$$

o/p of half adder

$$= C_h + C_{in} \times S_h$$

Logic Diagram of full adder using half-adders : -

